

1. which of the following can be represented for decoder?

- A) sequential circuit
- B) combinational circuit
- C) Logic Circuit
- D) None of the above

Ans: B) combinational circuit

2. Decoder converts ___ inputs to ___ outputs.

- A) 2^N , N
- B) N, 2^N
- C) N, 2N
- D) 2N, N

Ans: B) N , 2^N

3. Which type/s of stuck at fault model exhibit/s the reduced complexity level of test generation?

- A) Multiple
- B) Single
- C) Both A and B
- D) None of the above

Ans: A) Multiple

4. Which of the following is the application of decoder ?

- A) Converts analog audio to digital form
- B) Converts computer instructions to CPU control signal.
- C) Both A and B
- D) None of these

Ans: C) Both A and B

5. A 4 x 16 decoder can be constructed (with enable input) by :

- A) With five 2 x 4 decoders(each with enable inputs) only
- B) Using two 3 x 8 decoder(each with enable) only
- C) Both A and B
- (D) All of the above

Ans : A